

Miniserk Wiring Schematic

All power will be run off of a 3.7V LiPo Battery, check relevant links before wiring up TP4056, as the internal resistor might need to be swapped out, depending on LiPO mAh + amperage. Buttons should be tied low, make sure only to input 3.3V into GPIO pins, any higher can fry them. Speaker driver will obviously be wired to a speaker, check A4 documentation for reference. TODO: Power Toggle Switch.

